

# HP Z3801A GPS Receiver

## RS-422 to RS-232 Converter

### Interface options potpourri


Rev C  
5-21-2002

© COPYRIGHT 2001-2002 K8CU  
ALL RIGHTS RESERVED

DRAWN BY:	Bill Jones K8CU
PAGE	1 OF 1
DATE:	5-21-2002

Transformer is Jameco 104416 36 VAC@1.5 Amps  
\$8.95 [Http://www.jameco.com](http://www.jameco.com)

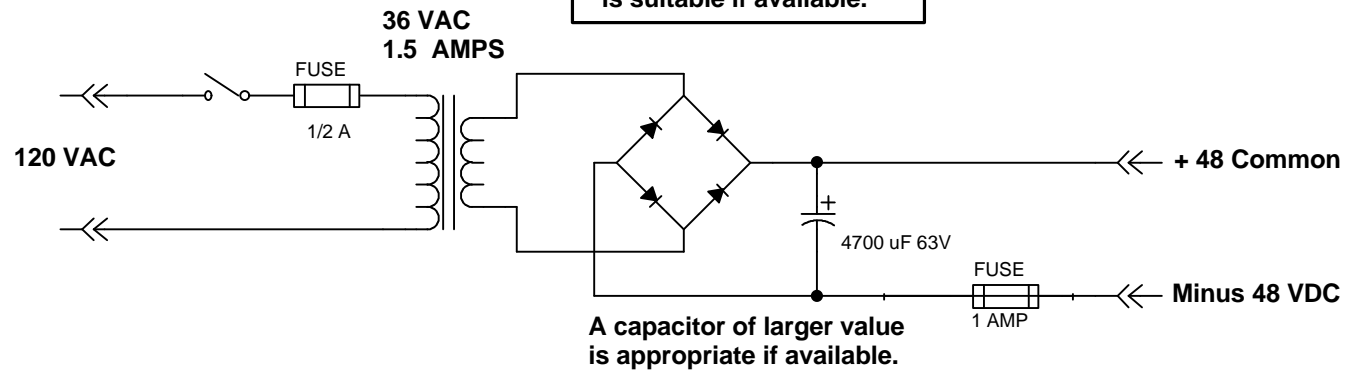Diode Bridge  
Minimum: 100 PIV 1 Amp  
100 PIV at 10 or more Amps  
is suitable if available.



*Voltage output is 54 VDC with no load.  
During oven warmup, output is 47 VDC.  
Expect 48-50 volts during normal operation.  
This meets HP power supply specifications  
for the -54 volt version Z3801A model.*

*A more costly regulated supply is not necessary.*

## HP Z3801A -48 VDC Power Supply

DRAWN BY: Bill Jones K8CU

PAGE 1 of 1

DATE: 5-21-2002



COPYRIGHT 2002 K8CU  
ALL RIGHTS RESERVED